



# Chapter 11

# Digital Logic

William Stallings, Computer Organization and Architecture, 9<sup>th</sup> Edition



# Objectives



- What are the basis of digital circuits?
- What are the basic electronic components?
- How can minimize a combinational circuits?
- After studying this chapter, you should be able to:
  - Understand the basic operations of Boolean algebra.
  - Use a Karnaugh map to simplify a Boolean expression.



# Contents



- 11.1- Boolean Algebra
- 11.2-Gates
- 11.3- Combinational Circuit



# 11.1- Boolean Algebra



- Mathematical discipline (môn) used to design and analyze the behavior of the digital circuitry in digital computers and other digital systems
- **Named after George Boole**
  - English mathematician
  - Proposed basic principles of the algebra in 1854
- Claude Shannon suggested Boolean algebra could be used to solve problems in relay-switching circuit design
- **Is a convenient tool:**
  - **Analysis**
    - It is an economical way of describing the function of digital circuitry
  - **Design**
    - Given a desired function, Boolean algebra can be applied to develop a simplified implementation of that function





# Boolean Algebra



- Investigated Set:

$$B = \{ \text{False}, \text{True} \} = \{ F, T \} = \{ 0, 1 \}$$

- Basic Operator: AND (.), OR (+), NOT

- Other operators: NAND (Not And), NOR (Not Or), XOR ( Exclusive OR)

- Representation:

$$\begin{aligned} A \text{ AND } B &= A \cdot B \\ A \text{ OR } B &= A + B \\ \text{NOT } A &= \overline{A} \end{aligned}$$

$$A + B \cdot C = A + (B \cdot C) = A + BC$$

$$\begin{aligned} A \text{ NAND } B &= \text{NOT}(A \text{ AND } B) = \overline{AB} \\ A \text{ NOR } B &= \text{NOT}(A \text{ OR } B) = \overline{A + B} \end{aligned}$$



# Boolean Variables and Operations



- **Makes use of variables and operations**

- Are logical
- A variable may take on the value 1 (TRUE) or 0 (FALSE)
- Basic logical operations are AND, OR, and NOT

- **AND**

- Yields true (binary value 1) if and only if both of its operands are true
- In the absence of parentheses the AND operation takes precedence over the OR operation
- When no ambiguity will occur the AND operation is represented by simple concatenation instead of the dot operator

- **OR**

- Yields true if either or both of its operands are true

- **NOT**

- Inverts the value of its operand

# Table 11.1- Boolean Operators

**Table 11.1** Boolean Operators

(a) Boolean Operators of Two Input Variables

<b>P</b>	<b>Q</b>	<b>NOT P</b> <b>(<math>\bar{P}</math>)</b>	<b>P AND Q</b> <b>(<math>P \cdot Q</math>)</b>	<b>P OR Q</b> <b>(<math>P + Q</math>)</b>	<b>P NAND Q</b> <b>(<math>\overline{P \cdot Q}</math>)</b>	<b>P NOR Q</b> <b>(<math>\overline{P + Q}</math>)</b>	<b>P XOR Q</b> <b>(<math>P \oplus Q</math>)</b>
0	0	1	0	0	1	1	0
0	1	1	0	1	1	0	1
1	0	0	0	1	1	0	1
1	1	0	1	1	0	0	0

(b) Boolean Operators Extended to More than Two Inputs (A, B, ...)

<b>Operation</b>	<b>Expression</b>	<b>Output = 1 if</b>
AND	$A \cdot B \cdot \dots$	All of the set {A, B, ...} are 1.
OR	$A + B + \dots$	Any of the set {A, B, ...} are 1.
NAND	$\overline{A \cdot B \cdot \dots}$	Any of the set {A, B, ...} are 0.
NOR	$\overline{A + B + \dots}$	All of the set {A, B, ...} are 0.
XOR	$A \oplus B \oplus \dots$	The set {A, B, ...} contains an odd number of ones.

# Table 11.2: Basic Identities of Boolean Algebra

**Table 11.2** Basic Identities of Boolean Algebra

Basic Postulates		
$A \cdot B = B \cdot A$	$A + B = B + A$	Commutative Laws
$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	$A + (B \cdot C) = (A + B) \cdot (A + C)$	Distributive Laws
$1 \cdot A = A$	$0 + A = A$	Identity Elements
$A \cdot \overline{A} = 0$	$A + \overline{A} = 1$	Inverse Elements
Other Identities		
$0 \cdot A = 0$	$1 + A = 1$	Associative Laws
$A \cdot A = A$	$A + A = A$	
$A \cdot (B \cdot C) = (A \cdot B) \cdot C$	$A + (B + C) = (A + B) + C$	DeMorgan's Theorem
$\overline{A \cdot B} = \overline{A} + \overline{B}$	$\overline{A + B} = \overline{A} \cdot \overline{B}$	





## 11.2- Basic Logic Gates

An electronic switch that is the elementary component of a digital circuit. It produces an electrical output signal that represents a binary 1 or 0 and is related to the states of one or more input signals by an operation of Boolean logic, such as AND, OR, or NOT (Microsoft Computer Dictionary)



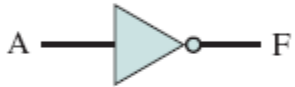

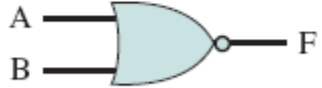

 
Name	Graphical Symbol	Algebraic Function	Truth Table															
AND		$F = A \cdot B$ or $F = AB$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	F	0	0	0	0	1	0	1	0	0	1	1	1
A	B	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = A + B$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	F	0	0	0	0	1	1	1	0	1	1	1	1
A	B	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOT		$F = \overline{A}$ or $F = A'$	<table><tr><th>A</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	F	0	1	1	0									
A	F																	
0	1																	
1	0																	
NAND		$F = \overline{AB}$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	F	0	0	1	0	1	1	1	0	1	1	1	0
A	B	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = \overline{A + B}$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	F	0	0	1	0	1	0	1	0	0	1	1	0
A	B	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
XOR		$F = A \oplus B$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	F	0	0	0	0	1	1	1	0	1	1	1	0
A	B	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																

Figure 11.1 Basic Logic Gates




## Uses of NAND Gates
 
## Uses of NOR Gates

 


**Figure 11.2** Some Uses of NAND Gates



**Figure 11.3** Some Uses of NOR Gates

# 11.3- Combinational Circuit



An interconnected set of gates whose output at any time is a function only of the input at that time

The appearance of the input is followed almost immediately by the appearance of the output, with only gate delays

Consists of  $n$  binary inputs and  $m$  binary outputs

## Can be defined in three ways:

- **Truth table**
  - For each of the  $2^n$  possible combinations of input signals, the binary value of each of the  $m$  output signals is listed
- **Graphical symbols**
  - The interconnected layout of gates is depicted
- **Boolean equations**
  - Each output signal is expressed as a Boolean function of its input signals

+

# Example: Using 3 ways for a Boolean Function of Three Variables

Sum of product (SOP)

$$F = \overline{A}B\overline{C} + \overline{A}BC + AB\overline{C}$$

Table 11.3 A Boolean Function of Three Variables

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

 


Figure 11.4 Sum-of-Products Implementation of Table 11.3

 


Figure 11.5 Product-of-Sums Implementation of Table 11.3

Product of Sum (POS)

$$F = (A + B + C) \cdot (A + B + \overline{C}) \cdot (\overline{A} + B + C) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + \overline{C})$$





# Algebraic Simplification

## Minimize a Boolean Function



- A Boolean function will be implemented as a combinational network → More complex function will cause a more complex network
- How to minimize a Boolean function?
  - Methods:
    - Karnaugh Map
    - Quine-McCluskey Method


# Algebraic Simplification

$$F = \overline{A}B\overline{C} + \overline{A}BC + AB\overline{C}$$

$$F = (A + B + C) \cdot (A + B + \overline{C}) \cdot (\overline{A} + B + C) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + \overline{C})$$

**Table 11.3** A Boolean Function of Three Variables

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

 

**Figure 11.6** Simplified Implementation

$$F = \overline{A}B\overline{C} + \overline{A}BC + AB\overline{C}$$

$$= \overline{A}B\overline{C} + \overline{A}BC + AB\overline{C} + \overline{A}B\overline{C}$$

$$= \overline{A}B\overline{C} + \overline{A}BC + AB\overline{C} + \overline{A}B\overline{C}$$


$$= \overline{A}B\overline{C} + AB\overline{C} + \overline{A}BC + \overline{A}B\overline{C}$$

$$= B\overline{C}(\overline{A} + A) + \overline{A}B(C + \overline{C})$$

$$= B\overline{C} + \overline{A}B$$

$$= B(\overline{A} + \overline{C})$$

# Karnaugh Map

 

**Figure 11.7** The Use of Karnaugh Maps to Represent Boolean Functions

- A convenient way of representing a Boolean function of a small number (up to four) of variables


 


Figure 11.8 The Use of Karnaugh Maps

Example


Karnaugh  
Maps

 



good

(a)  $F = \overline{A}B + B\overline{C}$

 

No good

(b)  $F = \overline{B}CD + ACD$

**Figure 11.9** Overlapping Groups

Overlapping


Groups

+

## Table 11.4- Truth Table for the One-Digit Packed Decimal Incrementer

**Table 11.4** Truth Table for the One-Digit Packed Decimal Incrementer

Number	Input				Number	Output			
	A	B	C	D		W	X	Y	Z
0	0	0	0	0	1	0	0	0	1
1	0	0	0	1	2	0	0	1	0
2	0	0	1	0	3	0	0	1	1
3	0	0	1	1	4	0	1	0	0
4	0	1	0	0	5	0	1	0	1
5	0	1	0	1	6	0	1	1	0
6	0	1	1	0	7	0	1	1	1
7	0	1	1	1	8	1	0	0	0
8	1	0	0	0	9	1	0	0	1
9	1	0	0	1	0	0	0	0	0
Don't care condition	1	0	1	0		d	d	d	d
	1	0	1	1		d	d	d	d
	1	1	0	0		d	d	d	d
	1	1	0	1		d	d	d	d
	1	1	1	0		d	d	d	d
	1	1	1	1		d	d	d	d

 

**Figure 11.10** Karnaugh Maps for the Incrementer

Figure

11.10

# Table 11.5: First Stage of Quine-McCluskey Method

**Table 11.5** First Stage of Quine-McCluskey Method

(for  $F = ABCD + AB\overline{C}D + AB\overline{C}\overline{D} + A\overline{B}CD + \overline{A}BCD + \overline{A}BC\overline{D} + \overline{A}B\overline{C}D + \overline{A}\overline{B}\overline{C}D$ )

	Product Term	Index	A	B	C	D	
0001	$\overline{A}\overline{B}\overline{C}D$	1	0	0	0	1	✓
0101	$\overline{A}B\overline{C}D$	5	0	1	0	1	✓
0110	$\overline{A}BC\overline{D}$	6	0	1	1	0	✓
1100	$AB\overline{C}\overline{D}$	12	1	1	0	0	✓
0111	$\overline{A}BCD$	7	0	1	1	1	✓
1011	$A\overline{B}CD$	11	1	0	1	1	✓
1101	$AB\overline{C}D$	13	1	1	0	1	✓
1111	$ABCD$	15	1	1	1	1	✓

$A \rightarrow 1, \text{Not } A \rightarrow 0$

$ABCD \rightarrow 1111 \rightarrow \text{Index}=15$



# Table 11.6: Last Stage of Quine-McCluskey Method

**Table 11.6** Last Stage of Quine-McCluskey Method  
(for  $F = ABCD + AB\bar{C}\bar{D} + AB\bar{C}D + A\bar{B}CD + \bar{A}BCD + \bar{A}BC\bar{D} + \bar{A}B\bar{C}D + \bar{A}\bar{B}\bar{C}D$ )

	$ABCD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$	$A\bar{B}CD$	$\bar{A}BCD$	$\bar{A}BC\bar{D}$	$\bar{A}B\bar{C}D$	$\bar{A}\bar{B}\bar{C}D$
$BD$	X	X			X		X	
$\bar{A}\bar{C}D$							<span style="border: 1px solid black;">X</span>	$\otimes$
$\bar{A}BC$					<span style="border: 1px solid black;">X</span>	$\otimes$		
$AB\bar{C}$		<span style="border: 1px solid black;">X</span>	$\otimes$					
$ACD$	<span style="border: 1px solid black;">X</span>			$\otimes$				

$$1111 + 1101 \rightarrow 11-1$$

$$0111 + 0101 \rightarrow 01-1$$

$$11-1 + 01-1 \rightarrow -1-1 \rightarrow BD$$



# Exercises

- 11.1** Construct a truth table for the following Boolean expressions:
- a.  $ABC + \overline{A}\overline{B}\overline{C}$
  - b.  $ABC + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C}$
  - c.  $A(\overline{B}\overline{C} + \overline{B}C)$
  - d.  $(A + B)(A + C)(\overline{A} + \overline{B})$
- 11.2** Simplify the following expressions according to the commutative law:
- a.  $A \cdot \overline{B} + \overline{B} \cdot A + C \cdot D \cdot E + \overline{C} \cdot D \cdot E + E \cdot \overline{C} \cdot D$
  - b.  $A \cdot B + A \cdot C + B \cdot A$
  - c.  $(L \cdot M \cdot N)(A \cdot B)(C \cdot D \cdot E)(M \cdot N \cdot L)$
  - d.  $F \cdot (K + R) + S \cdot V + W \cdot \overline{X} + V \cdot S + \overline{X} \cdot W + (R + K) \cdot F$
- 11.3** Apply DeMorgan's theorem to the following equations:
- a.  $F = \overline{V + \overline{A} + \overline{L}}$
  - b.  $F = \overline{\overline{A} + \overline{B} + \overline{C} + \overline{D}}$
- 11.4** Simplify the following expressions:
- a.  $A = S \cdot T + V \cdot W + R \cdot S \cdot T$
  - b.  $A = T \cdot U \cdot V + X \cdot Y + Y$
  - c.  $A = F \cdot (E + F + G)$
  - d.  $A = (P \cdot Q + R + S \cdot T)T \cdot S$
  - e.  $A = \overline{\overline{D} \cdot \overline{D} \cdot E}$
  - f.  $A = Y \cdot (W + X + \overline{\overline{Y} + \overline{Z}}) \cdot Z$
  - g.  $A = (B \cdot E + C + F) \cdot C$



# Summary

- 11.5** Construct the operation XOR from the basic Boolean operations AND, OR, and NOT.
- 11.6** Given a NOR gate and NOT gates, draw a logic diagram that will perform the three-input AND function.
- 11.7** Write the Boolean expression for a four-input **NAND gate**.
- 11.8** A combinational circuit is used to control a seven-segment display of decimal digits, as shown in Figure 11.35. The circuit has four inputs, which provide the four-bit code used in packed decimal representation ( $0_{10} = 0000, \dots, 9_{10} = 1001$ ). The seven outputs define which segments will be activated to display a given decimal digit. Note that some combinations of inputs and outputs are not needed.
  - a.** Develop a truth table for this circuit.
  - b.** Express the truth table in SOP form.
  - c.** Express the truth table in POS form.
  - d.** Provide a simplified expression.

+

# Summary

## Digital Logic

### Chapter 11

- Boolean Algebra
- Gates
- Combinational Circuit
  - **Algebraic Simplification**
    - Karnaugh Map
    - Quine-McCluskey Method